


Single element changes in electrical networks

Thomas Berger,
George Halikias and **Nicos Karcaniias** (City University London)


Institute of Mathematics, Ilmenau University of Technology

Berlin, February 17, 2012

Example: electrical RLC network

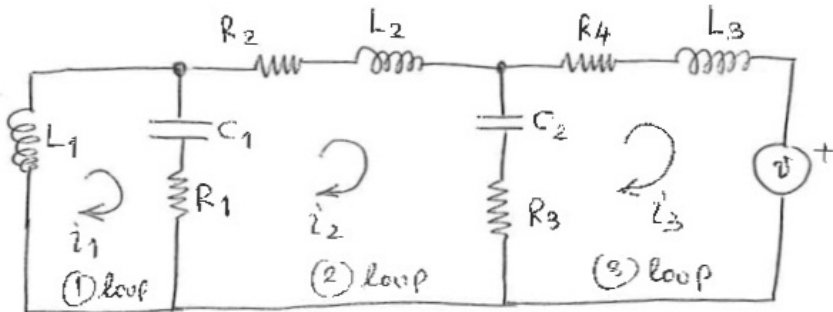

Example: electrical RLC network

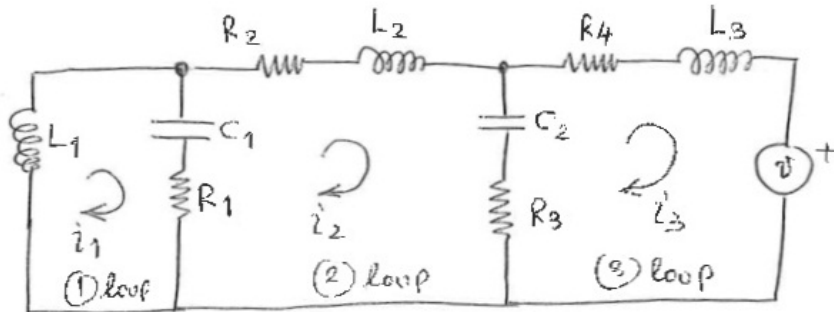

$$Z(s)i(s) = v_s(s),$$

$$Z(s) = s^{-1} \begin{bmatrix} \frac{1}{C_1} & -\frac{1}{C_1} & 0 \\ -\frac{1}{C_1} & \frac{1}{C_1} + \frac{1}{C_2} & -\frac{1}{C_2} \\ 0 & -\frac{1}{C_2} & \frac{1}{C_2} \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1 + R_2 + R_3 & -R_3 \\ 0 & -R_3 & R_3 + R_4 \end{bmatrix} + s \begin{bmatrix} L_1 & 0 & 0 \\ 0 & L_2 & 0 \\ 0 & 0 & L_3 \end{bmatrix}$$

RLC networks: impedance/admittance modeling

$$Z(s)i(s) = v_s(s), \quad Y(s)v(s) = i_s(s)$$

RLC networks: impedance/admittance modeling

$$Z(s)i(s) = v_s(s), \quad Y(s)v(s) = i_s(s)$$

$$Z(s), Y(s) : W(s) = sL + s^{-1}C + R$$

impedance modeling (loop analysis):

L : mass, spring, inductor

C : inertor, capacitor

R : damper, resistor

RLC networks: impedance/admittance modeling

$$Z(s)i(s) = v_s(s), \quad Y(s)v(s) = i_s(s)$$

$$Z(s), Y(s) : W(s) = sL + s^{-1}C + R$$

impedance modeling (loop analysis):

L : mass, spring, inductor

C : inertor, capacitor

R : damper, resistor

- element present in i -th loop (node) \Rightarrow its value is added to (i, i) position of the respective matrix
- element common to i -th and j -th loop (node) \Rightarrow its value is added to (i, i) and (j, j) positions, subtracted from (i, j) and (j, i) positions

Problem: effect of single element changes on the corresponding natural frequencies of the network

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$
becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^{\top}, G = G^{\top}$$

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$
becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^\top, G = G^\top$$

$$W(s) = s \begin{bmatrix} L_1 & 0 & 0 \\ 0 & L_2 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix}$$

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$
becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^\top, G = G^\top$$

$$W(s) = s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4+R_5 \end{bmatrix}$$

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$
becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^\top, G = G^\top$$

$$\begin{aligned} W(s) &= s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4+R_5 \end{bmatrix} \\ &= s \begin{bmatrix} L_1 & 0 & 0 \\ 0 & L_2 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix} \\ &\quad + sL_4(e_1 - e_2)(e_1 - e_2)^\top + R_5 e_3 e_3^\top \end{aligned}$$

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$ becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^\top, G = G^\top$$

$$\begin{aligned} W(s) &= s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4+R_5 \end{bmatrix} \\ &= s \begin{bmatrix} L_1 & 0 & 0 \\ 0 & L_2 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix} \\ &\quad + sL_4(e_1 - e_2)(e_1 - e_2)^\top + R_5e_3e_3^\top \\ &= s(F + L_4b_1b_1^\top) + (G + R_5b_2b_2^\top) \end{aligned}$$

Problem: effect of single element changes on the corresponding natural frequencies of the network

special cases: RC and RL networks $\rightarrow W(s) = sL + s^{-1}C + R$ becomes symmetric matrix pencil:

$$W(s) = \left\{ \begin{array}{l} \text{RL: } sL + R \\ \text{RC: } \hat{s}C + R, \hat{s} = s^{-1} \end{array} \right\} = sF + G, \quad F = F^\top, G = G^\top$$

$$\begin{aligned} W(s) &= s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4+R_5 \end{bmatrix} \\ &= s \begin{bmatrix} L_1 & 0 & 0 \\ 0 & L_2 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix} \\ &\quad + sL_4(e_1 - e_2)(e_1 - e_2)^\top + R_5e_3e_3^\top \\ &= s(F + L_4b_1b_1^\top) + (G + R_5b_2b_2^\top) \end{aligned}$$

here: $\boxed{\det(s(F + xbb^\top) + G)}$ $b = e_i$ or $b = e_i - e_j, i \neq j$

$$W(s) = s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix}$$

$$W(s) = s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix}$$

$$\det W(s) = \underbrace{\det W_{L_4=0}(s)}_{=p(s)} + sL_4z(s)$$

$$z(s) = ((sL_2 + R_2 + R_3)(sL_3 + R_3 + R_4) + sL_1(sL_3 + R_3 + R_4) - R_3^2)$$

$$W(s) = s \begin{bmatrix} L_1+L_4 & -L_4 & 0 \\ -L_4 & L_2+L_4 & 0 \\ 0 & 0 & L_3 \end{bmatrix} + \begin{bmatrix} R_1 & -R_1 & 0 \\ -R_1 & R_1+R_2+R_3 & -R_3 \\ 0 & -R_3 & R_3+R_4 \end{bmatrix}$$

$$\det W(s) = \underbrace{\det W_{L_4=0}(s)}_{=p(s)} + sL_4z(s)$$

$$z(s) = ((sL_2 + R_2 + R_3)(sL_3 + R_3 + R_4) + sL_1(sL_3 + R_3 + R_4) - R_3^2)$$

$$\det W(s) = 0 \iff 1 + L_4 \frac{sz(s)}{p(s)} = 0$$

Reformulation as root locus problem

[Binet-Cauchy-Theorem]

$$\begin{aligned}\det (s(F + xbb^\top) + G) &= \det \left([sF + G, I_k] \begin{bmatrix} I_k \\ sxbb^\top \end{bmatrix} \right) \\ &= g(s; F, G)^\top p(sx; b), \quad x \in \mathbb{R}\end{aligned}$$

Reformulation as root locus problem

[Binet-Cauchy-Theorem]

$$\begin{aligned}\det (s(F + xbb^\top) + G) &= \det \left([sF + G, I_k] \begin{bmatrix} I_k \\ sxbb^\top \end{bmatrix} \right) \\ &= g(s; F, G)^\top p(sx; b), \quad x \in \mathbb{R}\end{aligned}$$

$$\det (s(F + xbb^\top) + G) = \det(sF + G) + sx z(s; b)$$

root locus problem:

$$1 + x \frac{sz(s; b)}{\det(sF + G)} = 0$$

Theorem (Properties of the root locus)

$$1 + x \frac{s z(s; b)}{\det(sF + G)} = 0 \quad x \in \mathbb{R}, \quad \text{Assumption: } G \text{ is invertible}$$

- all branches of root locus are restricted to the real axis; for $x > 0$ all branches are restricted to the negative real axis

Theorem (Properties of the root locus)

$$1 + x \frac{s z(s; b)}{\det(sF + G)} = 0 \quad x \in \mathbb{R}, \quad \text{Assumption: } G \text{ is invertible}$$

- all branches of root locus are restricted to the real axis; for $x > 0$ all branches are restricted to the negative real axis
- $\exists p < 0 \exists \mu \in \mathbb{N}, \mu \geq 2 : \det(sF + G) = \eta(s)(s - p)^\mu \implies z(s; b) = \zeta(s)(s - p)^{\mu-1}$

Theorem (Properties of the root locus)

$$1 + x \frac{s z(s; b)}{\det(sF + G)} = 0 \quad x \in \mathbb{R}, \quad \text{Assumption: } G \text{ is invertible}$$

- all branches of root locus are restricted to the real axis; for $x > 0$ all branches are restricted to the negative real axis
- $\exists p < 0 \exists \mu \in \mathbb{N}, \mu \geq 2 : \det(sF + G) = \eta(s)(s - p)^\mu \implies z(s; b) = \zeta(s)(s - p)^{\mu-1}$
- $\text{rk}(F + bb^\top) = \text{rk } F + 1 \implies \deg \det(sF + G) = \deg z(s; b)$

Theorem (Properties of the root locus)

$$1 + x \frac{s z(s; b)}{\det(sF + G)} = 0 \quad x \in \mathbb{R}, \quad \textbf{Assumption: } G \text{ is invertible}$$

- all branches of root locus are restricted to the real axis; for $x > 0$ all branches are restricted to the negative real axis
- $\exists p < 0 \exists \mu \in \mathbb{N}, \mu \geq 2 : \det(sF + G) = \eta(s)(s - p)^\mu \implies z(s; b) = \zeta(s)(s - p)^{\mu-1}$
- $\text{rk}(F + bb^\top) = \text{rk } F + 1 \implies \deg \det(sF + G) = \deg z(s; b)$
- $\text{rk}(F + bb^\top) = \text{rk } F \implies \deg \det(sF + G) = \deg z(s; b) + 1$

$$F + xbb^T = \begin{bmatrix} C_1 + x & 0 \\ 0 & 0 \end{bmatrix}, \quad G = \begin{bmatrix} 1/R_1 & 0 \\ 0 & 1/R_2 \end{bmatrix}$$

$$F + xbb^T = \begin{bmatrix} C_1 + x & 0 \\ 0 & 0 \end{bmatrix}, \quad G = \begin{bmatrix} 1/R_1 & 0 \\ 0 & 1/R_2 \end{bmatrix}$$

$$\det(sF + G) + x \, sz(s; b) = 1/R_2(s(C_1 + x) + 1/R_1)$$

$$p(x) = -1/(R_1(C_1 + x)) :$$

$$F + xbb^T = \begin{bmatrix} C_1 + x & 0 \\ 0 & 0 \end{bmatrix}, \quad G = \begin{bmatrix} 1/R_1 & 0 \\ 0 & 1/R_2 \end{bmatrix}$$

$$\det(sF + G) + x \, sz(s; b) = 1/R_2(s(C_1 + x) + 1/R_1)$$

$$p(x) = -1/(R_1(C_1 + x)) :$$



$$\lim_{x \searrow -C_1} p(x) = -\infty$$

$$"p(-C_1) = \infty"$$

$$\lim_{x \rightarrow \infty} p(x) = 0$$


$$\lim_{x \nearrow -C_1} p(x) = \infty$$

$$"p(-C_1) = \infty"$$


Theorem (Behaviour of the root locus)

$x > 0$:

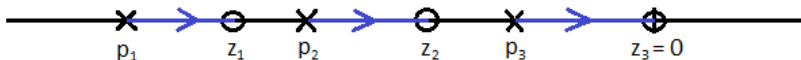- p pole of multiplicity $\mu \implies \mu$ or $\mu - 1$ of these poles do not change and at most one pole moves to the right
- \exists pole $p(x)$ s.t. $\lim_{x \rightarrow \infty} p(x) = 0$
- if $\text{rk}(F + bb^\top) = \text{rk } F$:



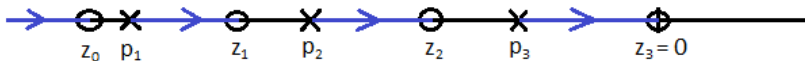- if $\text{rk}(F + bb^\top) = \text{rk } F + 1$, then an infinite pole becomes finite and moves to the right as x increases



$$F + xbb^T = \begin{bmatrix} C_1 & 0 \\ 0 & x \end{bmatrix}, \quad G = \begin{bmatrix} 1/R_1 & 0 \\ 0 & 1/R_2 \end{bmatrix}$$

$$F + xbb^T = \begin{bmatrix} C_1 & 0 \\ 0 & x \end{bmatrix}, \quad G = \begin{bmatrix} 1/R_1 & 0 \\ 0 & 1/R_2 \end{bmatrix}$$

$$\det(sF + G) + x sz(s; b) = (sC_1 + 1/R_1)(sx + 1/R_2)$$


$$\det(sF + G) = 1/R_2(sC_1 + 1/R_1) \implies p_1 = -1/(C_1 R_1)$$

$$sz(s) = sx(sC_1 + 1/R_1) \implies z_1 = -1/(C_1 R_1), \quad z_2 = 0$$



$x < 0$:

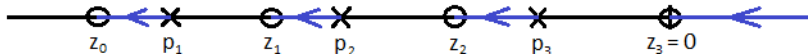- p pole of multiplicity $\mu \implies \mu$ or $\mu - 1$ of these poles do not change and at most one pole moves to the left
- if $\text{rk}(F + bb^\top) = \text{rk } F + 1$, then an infinite pole becomes finite and moves to the left on the positive real axis as x decreases, reaching 0 for $x \rightarrow -\infty$




- if $\text{rk}(F + bb^\top) = \text{rk } F$, then the smallest pole $p_1(x)$ moves to the left towards $-\infty$ and

$$\exists \kappa > 0 : \forall -\kappa < x < 0 : p_1(x) < p_1(0) \wedge \lim_{x \searrow -\kappa} p_1(x) = -\infty,$$

“ $p(-\kappa) = \infty$ ”,
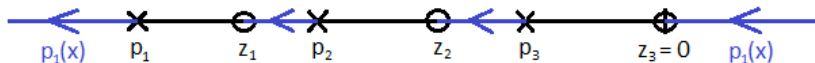
$$\forall x < -\kappa : p_1(x) > 0 \wedge \lim_{x \rightarrow -\infty} p_1(x) = 0$$



Summary

RLC networks: special cases of RC and RL → natural frequencies

Summary

RLC networks: special cases of RC and RL → natural frequencies

single element changes → root locus problem $1 + x \frac{s z(s; b)}{\det(sF + G)} = 0$

Summary

RLC networks: special cases of RC and RL \rightarrow natural frequencies

single element changes \rightarrow root locus problem $1 + x \frac{s z(s; b)}{\det(sF + G)} = 0$

- $x > 0$:
- all poles move to the right
 - if $\text{rk}(F + bb^\top) = \text{rk } F + 1$, then an infinite pole becomes finite
- $x < 0$:
- all poles move to the left
 - if $\text{rk}(F + bb^\top) = \text{rk } F + 1$, then an infinite pole becomes finite
 - if $\text{rk}(F + bb^\top) = \text{rk } F$, then a finite pole becomes infinite for a single value of x